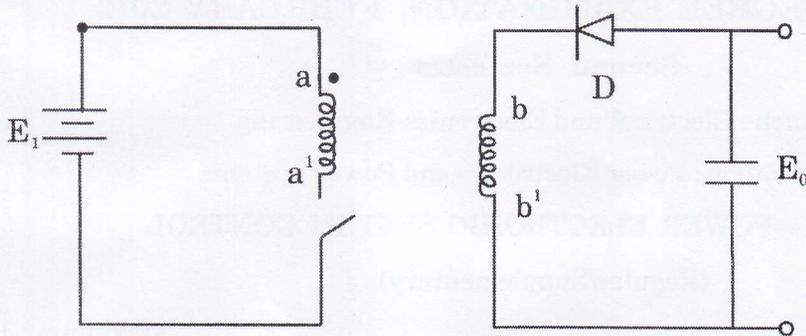


- (b) In the isolate converter of figure shown below $E_1 = 170$ V, Switching frequency = 20 kHz,



Duty cycle = 75%, Number of turns $naa' = 100$ number of turns $nbb' = 25$. Assume ideal components and repetitive conditions. Also consider continuous current through Diode D during OFF switch period. Calculate E_0 and Plot the waveform of voltage $V_{aa'}$ and $V_{bb'}$ considering relative magnitudes and time intervals. (12 marks)

6. (a) What is a flyback converter? Draw the circuit diagram and explain its principle of operation. (10 marks)
- (b) Draw the block schematic diagram of a Switched Mode Power Supply. (10 marks)
7. (a) What are resonant converters? How they are classified? (6 marks)
- (b) Discuss the principle of zero voltage and zero current switching. (6 marks)
- (c) Draw the circuit diagram of a Half bridge, Zero current switch-Quasi Resonant Converter. (8 marks)
- (5 × 20 = 100 marks)